

EECS 31L: INTRODUCTION TO DIGITAL DESIGN LAB LECTURE 5

Salma Elmalaki
salma.elmalaki@uci.edu

The Henry Samueli School of Engineering
Electrical Engineering and Computer Science
University of California, Irvine



LECTURE 5: LOGISTICS

- **All questions should be posted on canvas**
- Lab 3 is assigned —> You need to start early
- Lab 2 is currently being graded

LECTURE 5: LAST TIME

- Behavioral Description
- Sequential statements
 - if, case, for, while, ...
- Storage elements
- DFF
- JK FF
- Binary counters

LECTURE 5: OVERVIEW

- Blocking vs. non blocking assignment
- Structural description
- Binding and port instantiation
- Instantiation with GENERATE
- Structural with Delay
- Prepare for the midterm

LECTURE 5: OVERVIEW

- Blocking vs. non blocking assignment
- Structural description
- Binding and port instantiation
- Instantiation with GENERATE
- Structural with Delay
- Prepare for the midterm

BLOCKING VS. NON-BLOCKING ASSIGNMENT

Inside sequential block (like always or initial)

- **blocking**

- Use **=** operator
- The result of this assignment can be seen in the subsequent statements
- Statements are executed sequentially instead of concurrently

- **non-blocking**

- Use **<=** operator
- The result of this assignment cannot be seen in subsequent statements
- Statements are executed concurrently instead of sequentially
- The order of non-blocking assignments is not important as long as the destinations of the assignments are different signals

BLOCKING VS NON-BLOCKING

Blocking assignment: evaluation and assignment are immediate

```
always @ (a or b or c)
```

```
begin
```

```
  x = a | b;
```

1. Evaluate $a | b$, assign result to x

```
  y = a ^ b ^ c;
```

2. Evaluate a^b^c , assign result to y

```
  z = b & ~c;
```

3. Evaluate $b \& (\sim c)$, assign result to z

```
end
```

Non-Blocking assignment: all assignments are deferred until all right-hand sides have been evaluated (end of simulation timestep)

```
always @ (a or b or c)
```

```
begin
```

```
  x <= a | b;
```

1. Evaluate $a | b$ but defer assignment of x

```
  y <= a ^ b ^ c;
```

2. Evaluate a^b^c but defer assignment of y

```
  z <= b & ~c;
```

3. Evaluate $b \& (\sim c)$ but defer assignment of z

```
end
```

4. Assign x , y , and z with their new values

- Sometimes, as above, both produce the same result. Sometimes, not!

EXAMPLE; BLOCKING VS. NON-BLOCKING ASSIGNMENT

```
module block_nonblock();
reg a, b, c, d, e, f;
```

```
    // Blocking assignments
initial begin
    #10 a = 1'b1;
    #20 b = 1'b0;
    #40 c = 1'b1;
end
```


```
/* The simulator assigns
1 to a at time 10, 0 to
b at 30, and 1 to c at
70
*/
```

```
    // Non-blocking
    assignments
initial begin
    #10 d <= 1'b1;
    #20 e <= 1'b0;
    #40 f <= 1'b1;
end
endmodule
```


```
/* The simulator
assigns 1 to d at time
10, 0 to e at 20, and 1
to f at 40 */
```

 
EXAMPLE; BLOCKING VS. NON-BLOCKING ASSIGNMENT

```
module blocking (clk,a,c);
    input clk;
    input a;
    output c;
    wire clk,a;
    reg c,b;
    always @ (posedge clk )
    begin
        b = a;
        c = b;
    end
endmodule
```



```
module non-blocking (clk,a,c);
    input clk;
    input a;
    output c;
    wire clk,a;
    reg c,b;
    always @ (posedge clk )
    begin
        b <= a;
        c <= b;
    end
endmodule
```

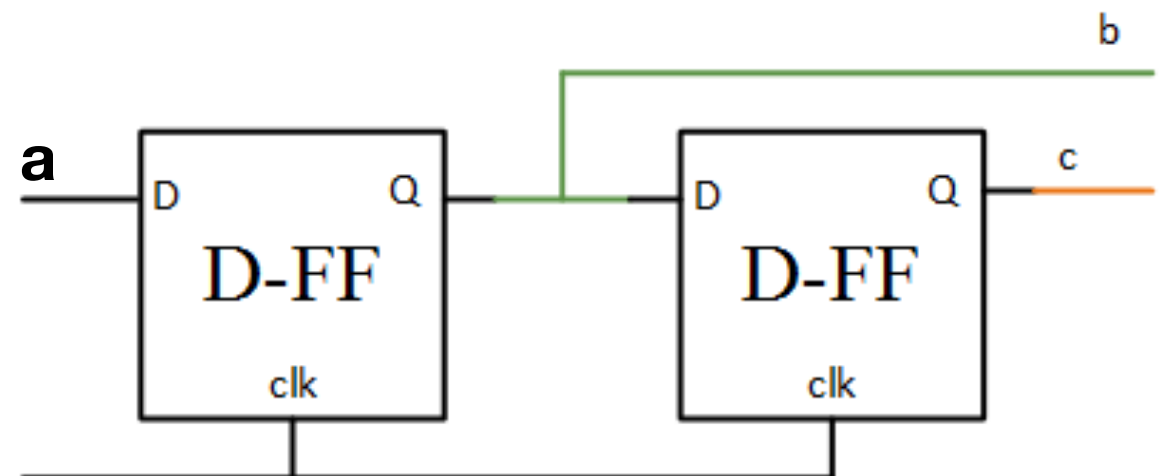

LECTURE 5: OVERVIEW

- Blocking vs. non blocking assignment
- Structural description
- Binding and port instantiation
- Instantiation with GENERATE
- Structural with Delay
- Prepare for the midterm

STRUCTURAL DESCRIPTION

- Best option when
 - Hardware details of the design are known
 - Schematic solution is available
- Structural description simulates the system by describing its **logical** components.
 - Components can be **gate level** (such as AND gates, OR gates, or NOT gates)
 - Components can be in a **higher logical level**, such as Register- Transfer Level (RTL) or processor level.
- Verilog **recognizes all the primitive gates**, such as AND, OR, XOR, NOT, and XNOR gates.
- Basic VHDL packages do not recognize any gates unless the package is linked to one or more libraries.

STRUCTURAL DESCRIPTION

Verilog Structural Description

```
module system(a,b,sum,cout);
```

```
    input a,b;
```

```
    output sum, cout;
```

```
    xor X1(sum, a, b); // (outputs, inputs) /* X1 is an optional identifier; it can be omitted.*/
```

```
    and a1(cout, a, b); /* a1 is optional identifier; it can be omitted.*/
```

```
endmodule
```

What if you want to build your primitive cell?

BINDING AND INSTANTIATION

```
module two (s1, s2, a1, b1);
    input a1;
    input b1;
    output s1, s2;
    xor (s1, a1, b1);
    and (s2, a1, b1);
endmodule
```

BINDING AND INSTANTIATION

Binding between two Modules in Verilog

```
module one( O1,O2,a,b);
    input [1:0] a;
    input [1:0] b;
    output [1:0] O1, O2;
```

```
two M0(O1[0], O2[0], a[0], b[0]); ←
two M1(O1[1], O2[1], a[1], b[1]); ←
endmodule
```

```
module two (s1, s2, a1, b1);
    input a1;
    input b1;
    output s1, s2;
    xor (s1, a1, b1);
    and (s2, a1, b1);
endmodule
```


Binds module **two to module **one****
The relationship as follows:

- O1[1] is the output of a two-input XOR gate with a[0] and b[0] as the inputs.
- O2[1] is the output of a two-input AND gate with a[1] and b[1] as the inputs.

Binds module **two to module **one****

- **Port Association**
 - Implicit by order (Position Mapping)

MODULE INSTANTIATION

 


```
/* Example
 * 1-bit FA module code
 */
```

```
module fulladder (input x, input y, input cin,
                  output sum, output cout);
wire m1, m2, m4, m7;
```

```
assign m1 = (~x & ~y & cin);
assign m2 = (~x & y & ~cin);
assign m4 = (x & ~y & ~cin);
assign m7 = (x & y & cin);
assign sum = m1 | m2 | m4 | m7;
assign cout = (x & y) | (cin & (x | y));
endmodule;
```

x	y	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

PORT INSTANTIATION

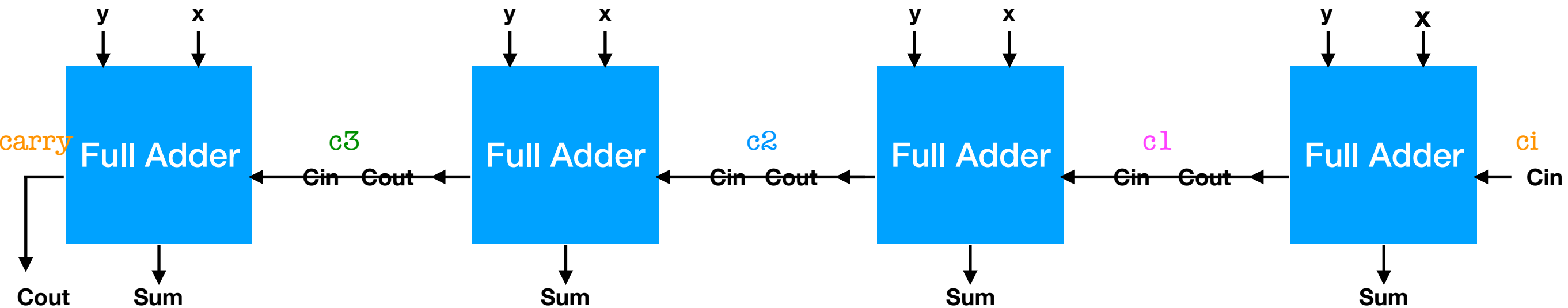

- Port Association

- Implicit by order (Position Mapping)
- Explicit by name (Nominal Mapping)

```
/* 1-bit FA module code */
module fulladder (input x, input y, input cin,
                  output sum, output cout);

wire m1, m2, m4, m7;


assign m1 = (~x & ~y & cin);
assign m2 = (~x & y & ~cin);
assign m4 = (x & ~y & ~cin);
assign m7 = (x & y & cin);
assign sum = m1 | m2 | m4 | m7;
assign cout = (x & y) | (cin & (x | y));
endmodule;
```

/* Implicit by Order */

```
module fa_4bit (result, carry, r1, r2, cin);
// input port declarations
input [3:0] r1 ;
input [3:0] r2 ;
input ci ;
// Output Port Declarations
output [3:0] result ;
output carry ;
wire c1, c2, c3;
fulladder u0 ( r1[0], r2[0], ci, result[0], c1 );
fulladder u1 ( r1[1], r2[1], c1, result[1], c2);
fulladder u2 ( r1[2], r2[2], c2, result[2], c3 );
fulladder u3 ( r1[3], r2[3], c3, result[3], carry );
endmodule;
```

The order of the ports match the instantiated module

PORT INSTANTIATION

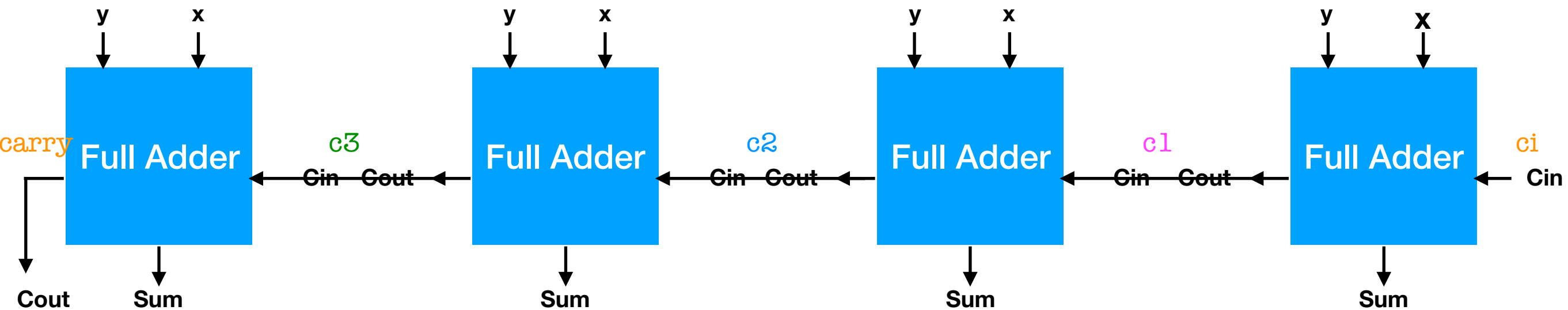

- Port Association
 - Implicit by order (Position Mapping)
 - Explicit by name (Nominal Mapping)

```

/* 1-bit FA module code */
module fulladder (input x, input y, input cin,
                  output sum, output cout);

wire m1, m2, m4, m7;

assign m1 = (~x & ~y & cin);
assign m2 = (~x & y & ~cin);
assign m4 = (x & ~y & ~cin);
assign m7 = (x & y & cin);
assign sum = m1 | m2 | m4 | m7;
assign cout = (x & y) | (cin & (x | y));
endmodule;
    
```

```

/* Explicit by name */
fulladder u0 (
    .x (r1[0]),
    .y (r2[0]),
    .cin (ci),
    .sum (result[0]),
    .cout (c1));
fulladder u1 (
    .x (r1[1]),
    .y (r2[1]),
    .cin (c1),
    .sum (result[1]),
    .cout (c2));
fulladder u2 (
    .x (r1[2]),
    .y (r2[2]),
    .cin (c2),
    .sum (result[2]),
    .cout (c3));
fulladder u3 (
    .x (r1[3]),
    .y (r2[3]),
    .cin (c3),
    .sum (result[3]),
    .cout (carry));
    
```

INSTANTIATION EXAMPLE OF GENERIC AND-GATE

Suppose you want to write a module to do this operation
 $c = \&a$

Verilog Generic and-gate

```
module and_gate (a,c);

input [4:0] a; output c;

wire [5:0] tmp;
assign tmp[0]=1'b1;
assign tmp[1] = tmp[0] & a[0];
assign tmp[2] = tmp[1] & a[1];
assign tmp[3] = tmp[2] & a[2];
assign tmp[4] = tmp[3] & a[3];
assign tmp[5] = tmp[4] & a[4];
assign c = (tmp[5]==1'b1)?1'b1:1'b0;
endmodule
```

Do you see a pattern?

What if you want to design a generic module with arbitrary size of input a?

INSTANTIATION EXAMPLE OF GENERIC AND-GATE

Verilog Generic and-gate

```

module and_gate (a,c);
parameter N=2;
input [N-1:0] a; output c;

wire [N:0] tmp;
assign tmp[0]=1'b1;

genvar i;
generate
for (i=0;i<N;i=i+1)
begin
    assign tmp[i+1]=tmp[i]&a[i];
end
endgenerate
assign c = (tmp[N]==1'b1)?1'b1:1'b0;
endmodule

```

Verilog and-gate instantiation

```

module testbench();
parameter N=4;
reg [N-1:0] in_tb;
wire c_tb;

and_gate #(N) instant (.a(in_tb),
                        .c(c_tb)
                        );

initial
begin
    in_tb=&1'b1;
end


always
begin
    //rest of test bench

```


LECTURE 5: OVERVIEW

- Blocking vs. non blocking assignment
- Structural description
- Binding and port instantiation
- Instantiation with GENERATE
- Structural with Delay
- Prepare for the midterm

 INSTANTIATION EXAMPLE OF SHIFT REGISTER WITH LOAD



Four bit shift register

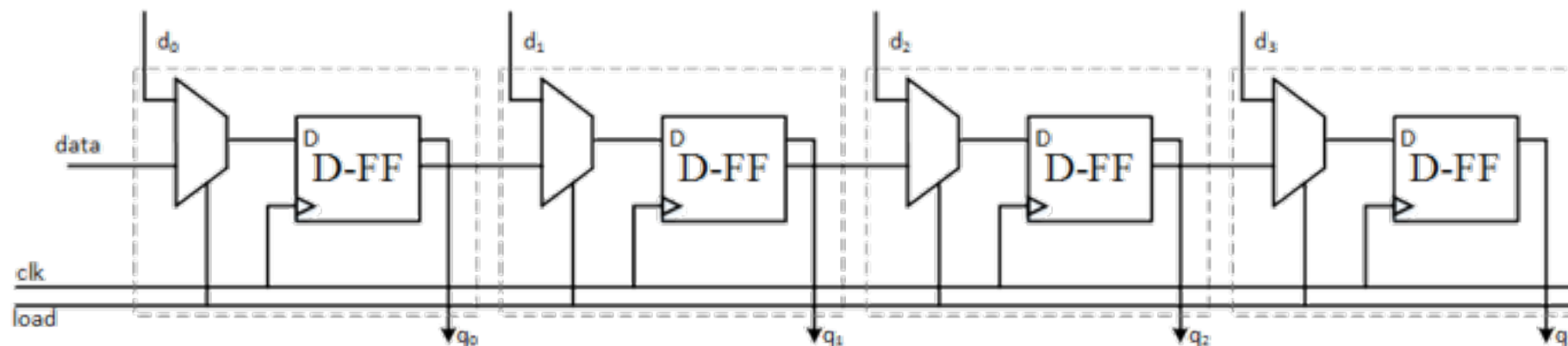


INSTANTIATION EXAMPLE OF SHIFT REGISTER WITH LOAD

Verilog standard cell

```
module shift_reg_cell (a,b,load,clk,q);

input  a,b,load,clk;
output reg q;

 
always @ (posedge clk)
begin
if (load==1'b1)
    q=a;
else
    q=b;
end
endmodule
```



Verilog shift register

```
module shift_reg (data,clk,load,d,q);
input  data,clk,load;
input [0:3] d;
output [0:3] q;
```
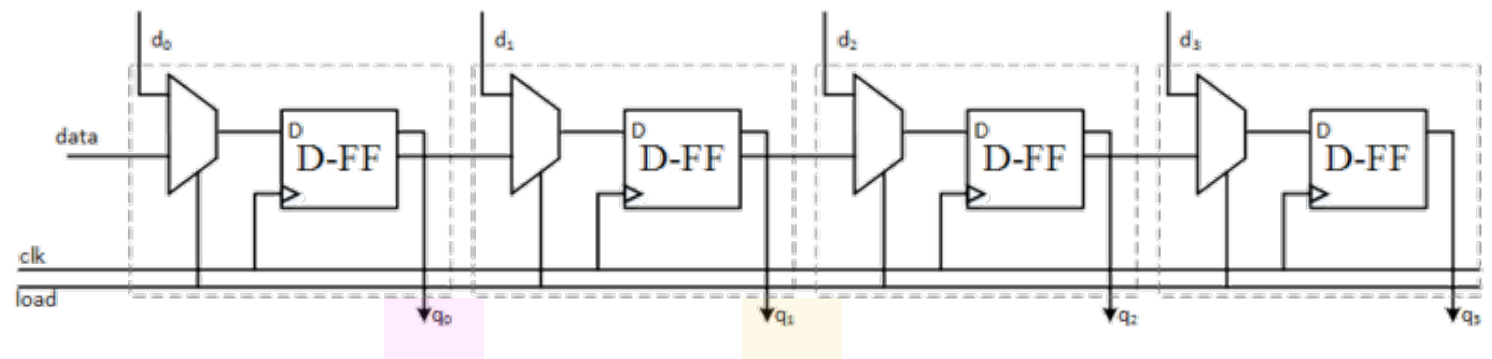
```
    shift_reg_cell DFF0(.a(d[0]),.b(data),.load(load),.clk(clk),.q(q[0]));
    shift_reg_cell DFF1(.a(d[1]),.b(q[0]),.load(load),.clk(clk),.q(q[1]));
    shift_reg_cell DFF2(.a(d[2]),.b(q[1]),.load(load),.clk(clk),.q(q[2]));
    shift_reg_cell DFF3(.a(d[3]),.b(q[2]),.load(load),.clk(clk),.q(q[3]));
endmodule
```




INSTANTIATION EXAMPLE OF SHIFT REGISTER WITH LOAD (GENERATE)

Verilog-standard cell

```
module shift_reg_cell (a,b,load,clk,q);
```

```
input  a,b,load,clk;
output reg q;
```
 
```
always @ (posedge clk)
begin
if (load==1'b1)
    q=a;
else
    q=b;
end
endmodule
```



Verilog-shift register

```
module shift_reg (data,clk,load,d,q);
```

```
input  data,clk,load;
input  [0:3] d;
output [0:3] q;
```

```
shift_reg_cell DFF0 (.a(d[0]),.b(data),.load(load),.clk(clk),.q(q[0]));
```

```
genvar i
```

```
generate
```

```
for (i=1; i<4;i=i+1)
```


```
begin
```

```
    shift_reg_cell OTHERS (.a(d[i]),.b(q[i-1]),.load(load),.clk(clk),.q(q[i]));
```

```
end
```

```
endgenerate
```

```
endmodule
```

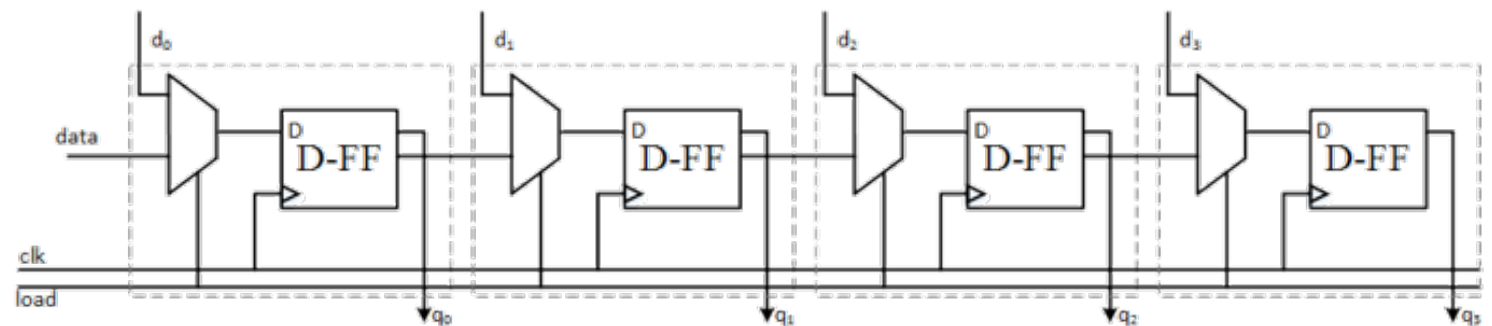

INSTANTIATION EXAMPLE OF SHIFT REGISTER WITH LOAD (**GENERATE**)

N-bit Shift Register

```

module shift_reg (data,clk,load,d,q);
input  data,clk,load;
input  [0: N] d;
output [0: N] q;
parameter N = 4
shift_reg_cell DFF0(.a(d[0]),.b(data),.load(load),.clk(clk),.q(q[0]));
genvar i
generate
for (i=1; i<N;i=i+1)
begin
    shift_reg_cell OTHERS (.a(d[i]),.b(q[i-1]),.load(load),.clk(clk),.q(q[i]));
end
endgenerate
endmodule

```

The change you need to make a generic shift register

LECTURE 5: OVERVIEW

- Blocking vs. non blocking assignment
- Structural description
- Binding and port instantiation
- Instantiation with GENERATE
- Structural with Delay
- Prepare for the midterm



Break 10 minutes



EXAMPLE OF 1-BIT MUX 2_1 (WITH DELAY) FROM LECTURE 3

- 2x1 multiplexer
 - with active low enable
 - with constant delay
 - All gate delays are 7 ns

Input		Output
SEL	Gbar	Y
X	1	0
0	0	A
1	0	B

 
 


EXAMPLE OF 1-BIT MUX 2_1 (WITH DELAY) FROM LECTURE 3

```

module mux_enable(a,b,sel,gbar,y)
  input a,b,sel,gbar;
  output y;
  wire s1,s2,s3,s4,s5;
  time dly = 7; //simulation screen units
  assign #dly y=s4|s5;
  assign #dly s4=a & s2 & s1;
  assign #dly s5=b & s3 & s1;
  assign #dly s2= ~sel;
  assign #dly s3= ~s2;
  assign #dly s1= ~gbar;
endmodule

```

 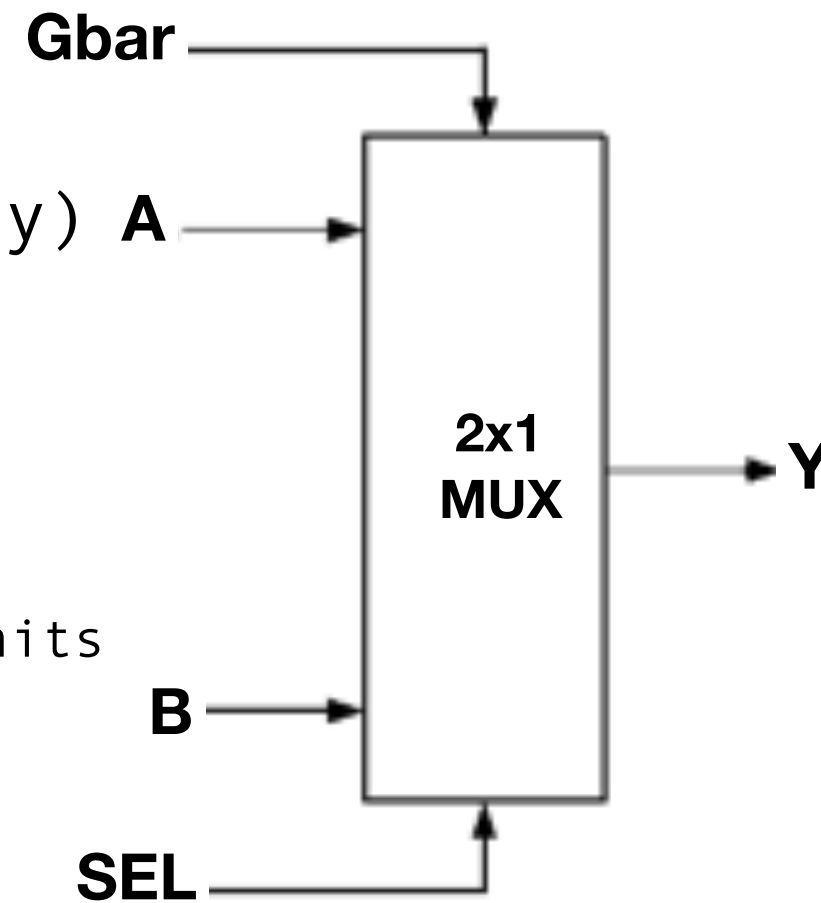

STRUCTURAL DESCRIPTION OF 1-BIT MUX 2_1 (WITH DELAY)

- MUX 2_1 (See lecture 3)

- Not gates

- 0 delay
- 7ns delay

- And gate


- 2 inputs, 0 delay
- 2 inputs, 7ns delay
- 3 inputs, 0 delay
- 3 inputs, 7ns delay

- Or gate

- 2 inputs, 0 delay
- 2 inputs, 7ns delay
- 3 inputs, 0 delay
- 3 inputs, 7ns delay

- Xor gate

- 2 inputs, 0 delay

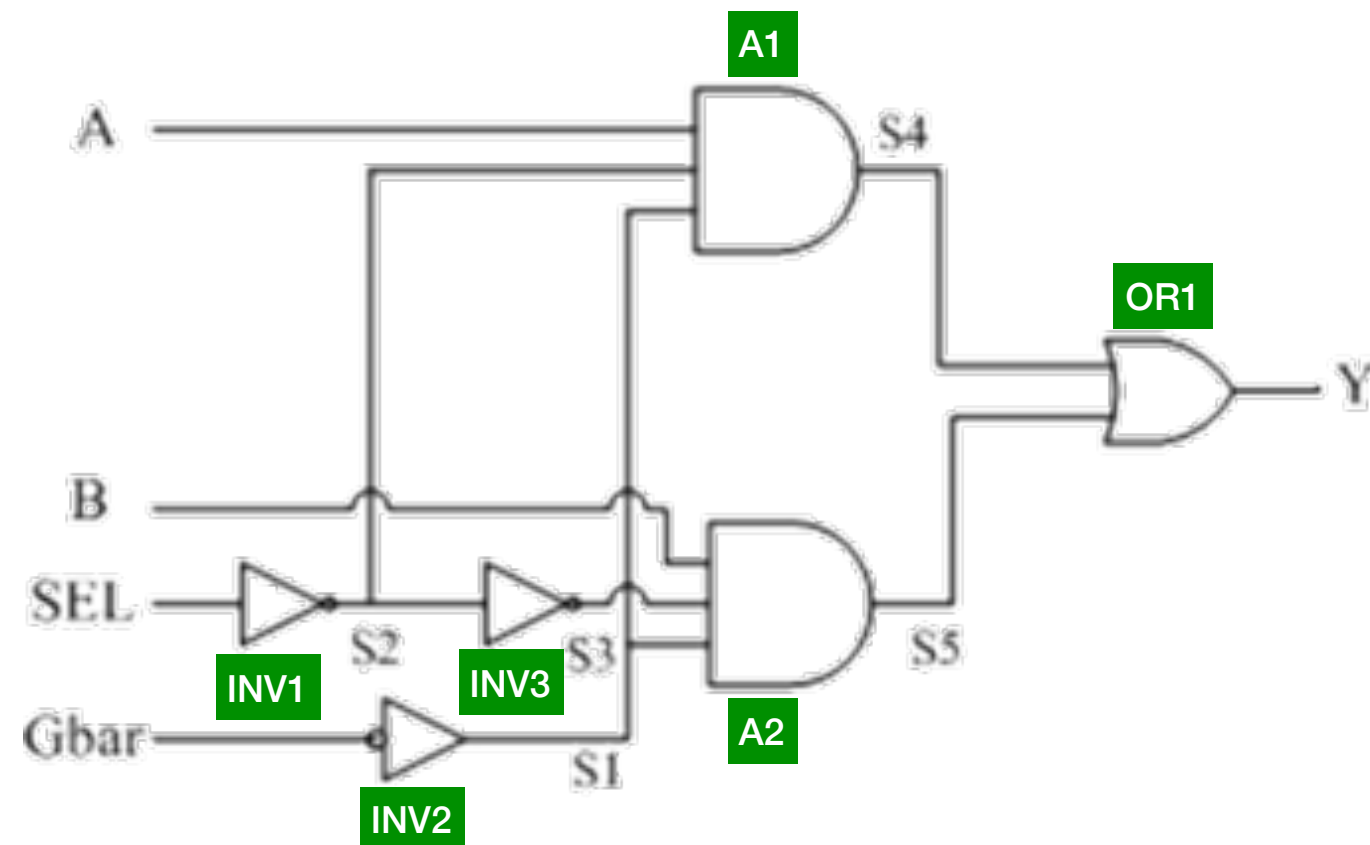

Instance	delay
INV1, INV3	7ns
INV2	0ns
A1,A2	7ns
OR1	7ns

STRUCTURAL DESCRIPTION OF 1-BIT MUX 2_1 (WITH DELAY)

```

module mux2x1 (a,b,sel,gbar,y);
input  a,b,sel,gbar;
output wire y; // no need to be defined as output reg y

wire s1,s2,s3,s4,s5;


and #7 (s4,a,s2,s1); /* the red ones, the first relates
to output*/
or #7 (y,s4,s5);
and #7 (s5,b,s3,s1);
not #7 (s2,sel);
not #7 (s3,s2);
not (s1,gbar);

endmodule

```

why?

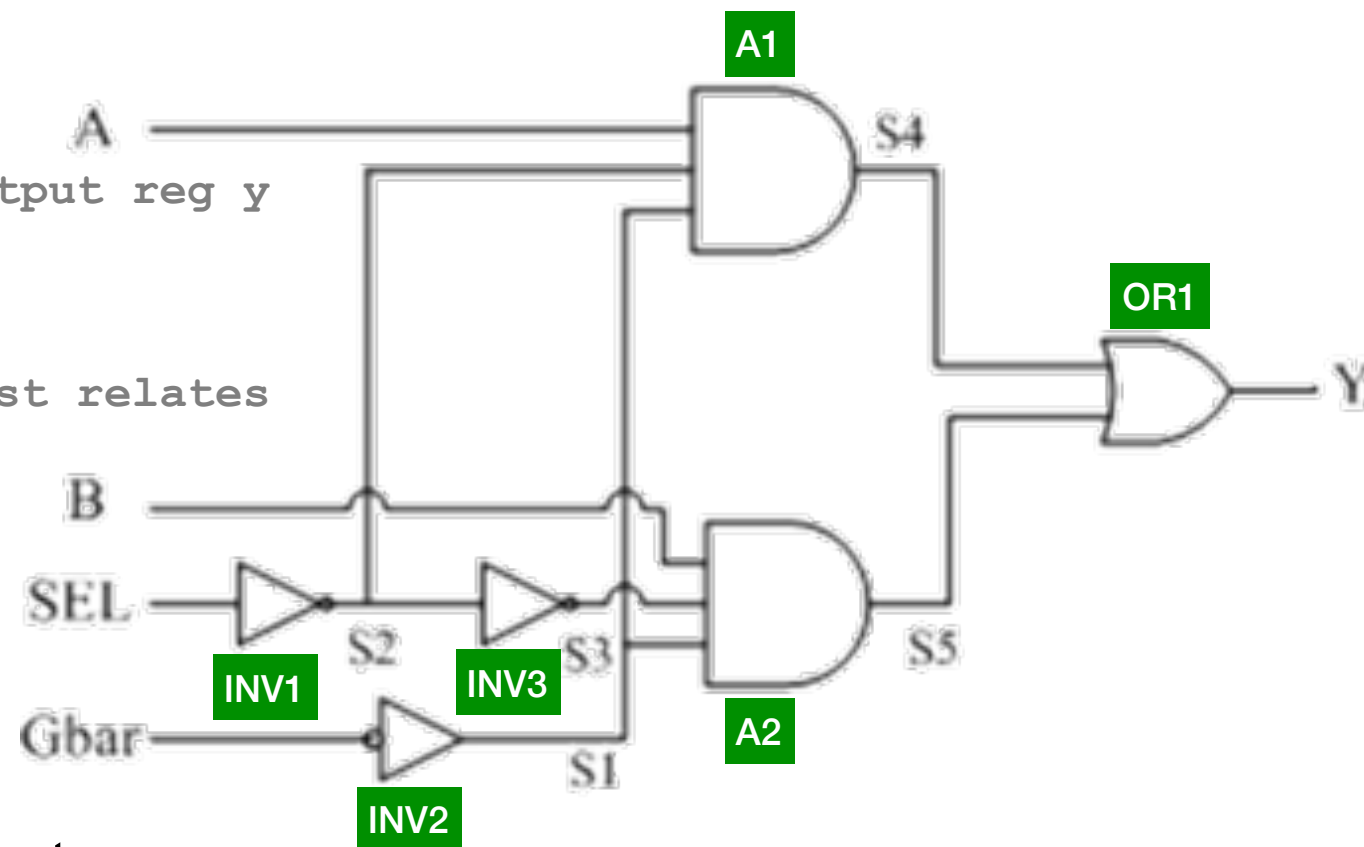Because all the assignments are concurrent in structural, so the y should be net type not reg type



Instance	delay
INV1, INV3	7ns
INV2	0ns
A1,A2	7ns
OR1	7ns

LECTURE 5: OVERVIEW

- Blocking vs. non blocking assignment
- Structural description
- Binding and port instantiation
- Instantiation with GENERATE
- Structural with Delay
- Prepare for the midterm - Last year midterm will be posted

PREPARE FOR THE MIDTERM

- Differences between the three types of design description:
 - Dataflow
 - Behavioral
 - Structural
- Assignment with delays in concurrent execution
- Difference between concurrent and sequential execution
- Blocking vs. non blocking
- Common mistakes in Verilog
- How to write a testbench (initial block, simulate a clock, ...)

QUESTIONS