

EECS 31L: INTRODUCTION TO DIGITAL DESIGN LAB LECTURE 3

Salma Elmalaki
salma.elmalaki@uci.edu

The Henry Samueli School of Engineering
Electrical Engineering and Computer Science
University of California, Irvine



LECTURE 3: LOGISTICS

- **All questions should be posted on canvas**
- Lab 3 deadline is Monday 2/1/2021 at 11:00 pm on canvas
 - No late submission will be considered
- For Mac users, install VMs for emergencies
- Copying files from the server you can use:

```
scp username@hostname:/path/to/remote/file /path/to/local/file
```

LECTURE 3: OVERVIEW

- Typical mistakes in Verilog
- Data flow description
- Concurrent signal assignment + examples
- Assignment with delay + examples
- Concurrent code Verilog

LECTURE 3: OVERVIEW

- Typical mistakes in Verilog
- Data flow description
- Concurrent signal assignment + examples
- Assignment with delay + examples
- Concurrent code Verilog

TYPICAL MISTAKES IN VERILOG

```
module mult_comb (a, b, P)
```

Semicolon (;) is missing at the end of the statement

```
input [1:0] A, b;
```

'A' is not defined; it should be lowercase

```
output (3:0) P;
```

Brackets [3:0] should be used instead of parenthesis

```
P[0] = a[0] and b[0];
```

The word 'assign' is missing; The word 'and' cannot be used in verilog. The logical operator "&" should be used

```
Assign p[0] = S[0] | a[0];
```

S[0] is a vector and not declared; 'assign' is a lowercase

```
endmodule;
```

No semicolon (;) at the end of 'endmodule'

TYPICAL MISTAKES IN VERILOG

```
reg out;

always @(a,b) begin
    out = a & b;
end
```

```
reg out2;

always @(a,b) begin
    assign out2 = a ^ b;
end
```

There is no 'assign' keyword in always blocks!

TYPICAL MISTAKES IN VERILOG

```
module ...
```

```
•  
•  
•
```

```
always @(a,b) begin
```

```
    x = a^b
```

```
end
```

```
always @(reset) begin
```

```
    x = 1'b0;
```


```
end
```

```
endmodule
```

Setting the same **reg** in multiple **always** blocks


- Simulators will typically do what you tell them to do
- Synthesis tools will typically give a warning
- Never do this in Hardware verilog
- You might be able to get away with it in testing verilog but normally don't do it

TYPICAL MISTAKES IN VERILOG

 

```
always @(a) begin // missing b
    out = a & b;
end
```

Result

 

Incomplete Sensitivity List

- *out* updates when *a* changes as expected
- *out* does not update when *b* changes!
- Put another way, *b* can change all it wants but *out* will not update - this requires a memory element to remember the last value of *out*
- Synthesis tool will give you a warning
- Using the construct:
`always @(*)`
 eliminates this type of bug₈

TYPICAL MISTAKES IN VERILOG

```
wire a;
```

```
wire [3:0] b;
```

Why are the assignments below illegal?

```
assign b(4) = a;
```

Wrong Indexing

- Order (ascending or descending) is reversed
- Incorrect use of parenthesis
- Index values fall outside the actual range

LECTURE 3: OVERVIEW

- Typical mistakes in Verilog
- Data flow description
- Concurrent signal assignment + examples
- Assignment with delay + examples
- Concurrent code Verilog

DATA FLOW DESCRIPTION

- How data flows from input to output
- Circuit is designed with **concurrent** statements
 - The order of the statements is **not** important
 - The execution of the statements is event-based
 - Useful for combinational circuits modeling
- More realistic circuit modeling if either of the followings are available:
 - The Boolean equation
 - Truth table

DATA FLOW DESCRIPTION

- All ports are defined as **wires** by default
 - output ports defined as reg to be used inside **sequential** blocks
- In concurrent assignment, **assign to a wire**



```
input a, b;
```

```
reg tmp; // tmp should be defined as wire
```

```
assign temp = a & b; // syntax error
```

DATA FLOW DESCRIPTION - EXAMPLE 1

  - AND-OR block
- The circuit of the design



- A Boolean function of the output

$$\Rightarrow y = (ab) + (cd)$$

| Input | | | | Output |
|-------|---|---|---|--------|
| a | b | c | d | Y |
| 1 | 1 | - | - | 1 |
| - | - | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 |


VERILOG CODE FOR AND-OR BLOCK

```
module and_or(a,b,c,d,y);
    input a,b,c,d;
    output y;
```

```
    wire s1,s2;
    assign s1 = a & b;
    assign s2 = c & d;
    assign y = s1 | s2;
endmodule
```

Wire statement here is not necessarily needed since s1 and s2 are single bit

Runs concurrently

 


| Input | | | | Output |
|-------|---|---|---|--------|
| a | b | c | d | Y |
| 1 | 1 | - | - | 1 |
| - | - | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 |

VERILOG CODE FOR AND-OR BLOCK

```
module and_or(a,b,c,d,y);
    input a,b,c,d;
    output y;
```

```
    wire s1,s2;
    assign s1 = a & b;
    assign s2 = c & d;
    assign y  = s1 | s2;
endmodule
```

Runs concurrently

 


| Input | | | | Output |
|-------|---|---|---|--------|
| a | b | c | d | Y |
| 1 | 1 | - | - | 1 |
| - | - | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 |

VERILOG CODE FOR AND-OR BLOCK

```
module and_or(a,b,c,d,y);
    input a,b,c,d;
    output y;
```

```
    wire s1,s2;
    assign y = s1 | s2;
    assign s2 = c & d;
    assign s1 = a & b;
endmodule
```

Runs concurrently

 

| Input | | | | Output |
|-------|---|---|---|--------|
| a | b | c | d | Y |
| 1 | 1 | - | - | 1 |
| - | - | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 |

CONCURRENT SIGNAL ASSIGNMENT (CONT'D)

- Signal assignment execution
 - Different from language such as C
 - An event should occur on the right side
 - Event is a change of value of right side
 - For example, from 0 to 1 or even 0 to Z
 - The statement that receives an event is executed first
 - More than one statement can have event at the same time
 - executed concurrently
- Signal statement phases
 - Calculation
 - At the time of event happens
 - Assignment
 - After calculation is done
- **assign** is the keyword

SIMULATION OF AND-OR

• Event at T_0

- On a and b; statement 1 is executed.
- After executing first statement the output s1 is updated
 - No delay; there is an event on the third statement at T_0
 - So y also changes at T_0


• Event at T_1

- On a, c and d
- Statement 1 and 2 executed first
- No delay; statement 3 executed
- S_1 and S_2 are updated

• Event at T_2

- On c; statement 2 executed

```
assign s1 = a & b;
assign s2 = c & d;
assign y  = s1 | s2;
```

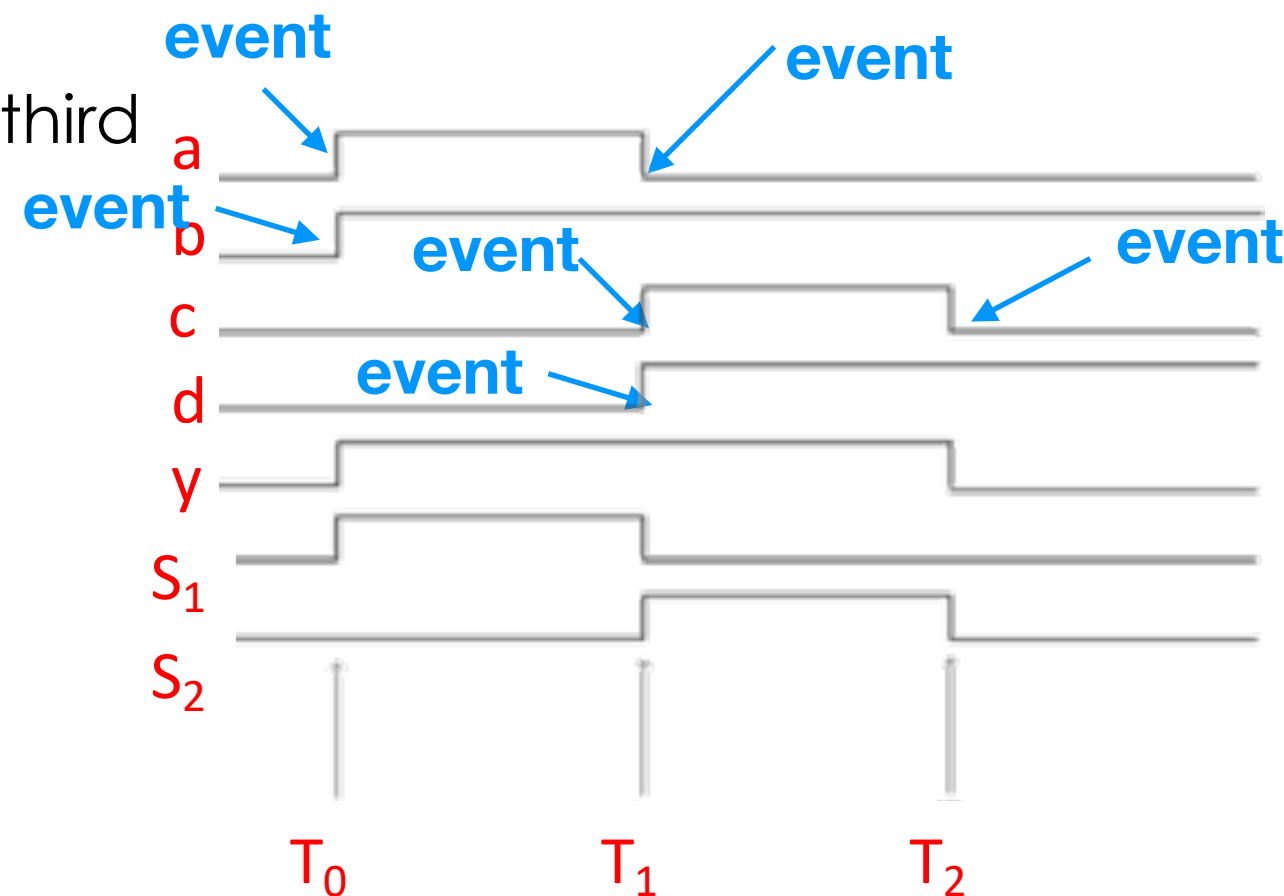

LECTURE 3: OVERVIEW

- Typical mistakes in Verilog
- Data flow description
- Concurrent signal assignment + examples
- Assignment with delay + examples
- Concurrent code Verilog

CONSTANT DECLARATION

- Has same usage as other languages

- Declared by its type such as integer or time
- Use **=** to assign it a value
- the unit is simulation screen unit

```
time period =100; //verilog
parameter period = 100;
`define period 100;
```

- More data types:

- **integer** - 4-state Verilog data type, 32-bit signed integer
- **time** - 4-state Verilog data type, 64-bit unsigned integer

- Delay assignment

- Use #

```
assign #10 S1 = a & b;
```

AND-OR BLOCK WITH DELAY

```
module and_or(a,b,c,d,y);
    input a,b,c,d;
    output y;


    wire s1,s2;
    time dly = 10;
    assign #dly s1 = a & b;
    assign #dly s2 = c & d;
    assign #dly y  = s1 | s2;
endmodule
```

SIMULATION OF AND-OR BLOCK WITH DELAY

• Event at T_0

- On a and b; statement 1 is executed
- After dly (at T_1) S_1 is updated;
- Statement 3 is executed
- After dly (at T_2) y is updated

```
assign #dly s1 = a & b;
assign #dly s2 = c & d;
assign #dly y  = s1 | s2
```

 

SIMULATION OF AND-OR BLOCK WITH DELAY


• Event at T_0

- On a and b; statement 1 is executed
- After dly (at T_1) S_1 is updated;
- Statement 3 is executed
- After dly (at T_2) y is updated

```
assign #dly s1 = a & b;
assign #dly s2 = c & d;
assign #dly y  = s1 | s2
```

• Event at T_3

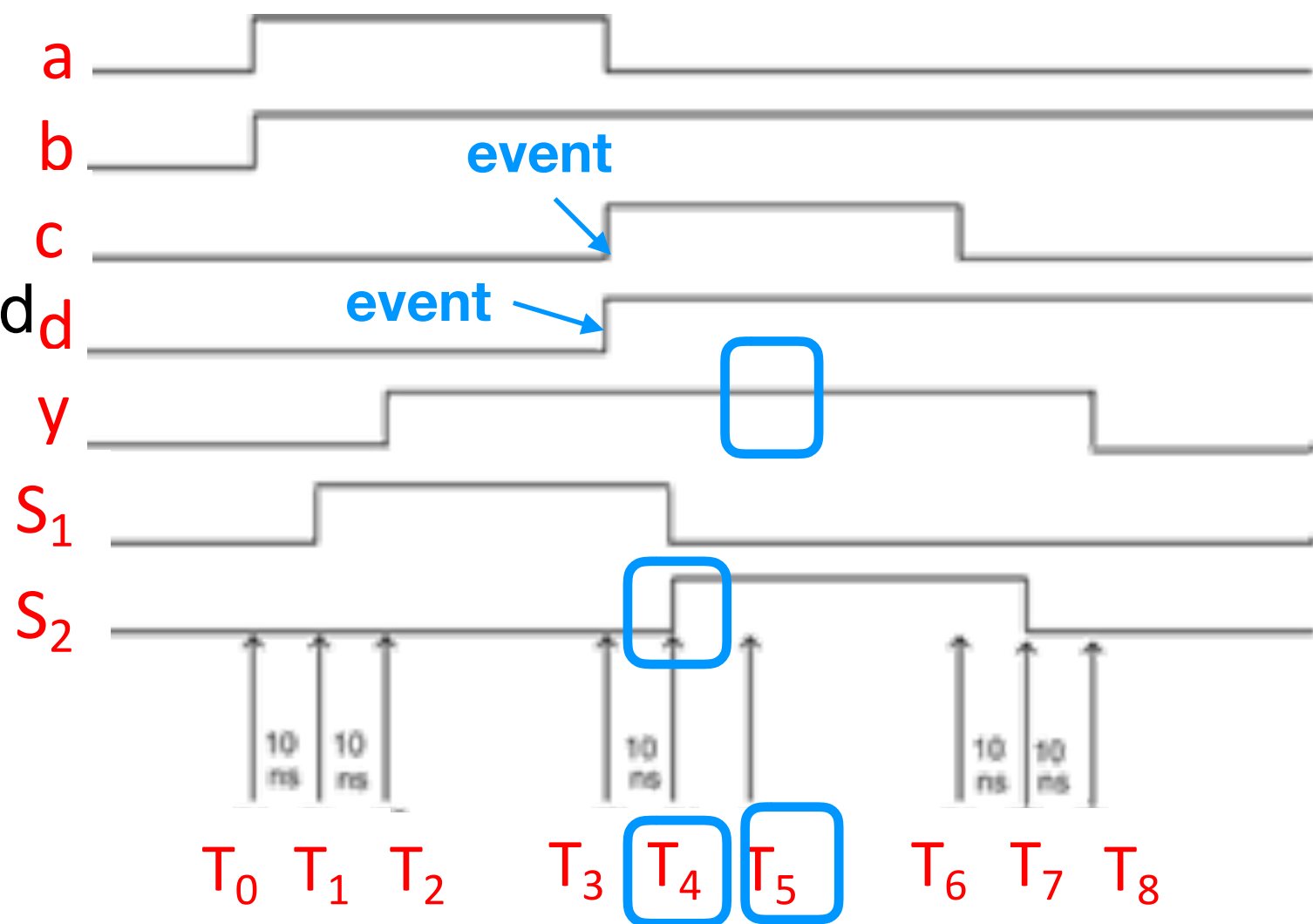- On a, c and d;
- Statement 1 & 2 are executed
- At T_4 , S_1 & S_2 are updated
- Statement 3 is executed
- At T_5 , y is updated



SIMULATION OF AND-OR BLOCK WITH DELAY

• Event at T_0

- On a and b; statement 1 is executed
- After dly (at T_1) S_1 is updated;
- Statement 3 is executed
- After dly (at T_2) y is updated


```
assign #dly s1 = a & b;
assign #dly s2 = c & d;
assign #dly y  = s1 | s2
```

• Event at T_3

- On a, c and d;
- Statement 1 & 2 are executed
- At T_4 , S_1 & S_2 are updated
- Statement 3 is executed
- At T_5 , y is updated

• Event at T_6


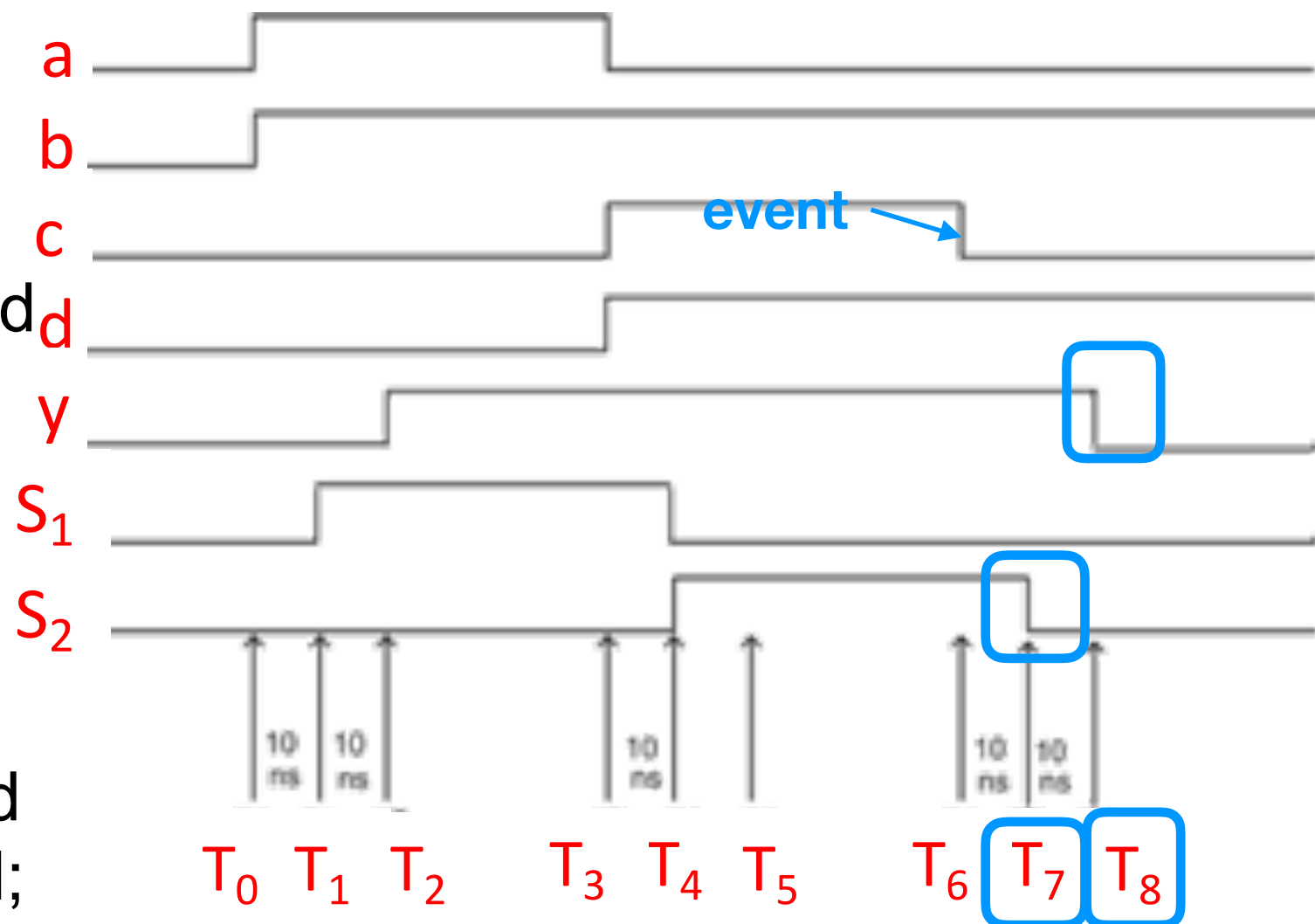
- on c; statement 2 is executed
- after dly (at T_7) S_1 is updated;
- statement 3 is executed
- after dly (at T_8) y is updated



DATA FLOW DESCRIPTION OF MUX 2X1

- 2x1 multiplexer
 - with active low enable
 - with constant delay
 - All gate delays are 7 ns



| Input | | Output |
|-------|------|--------|
| SEL | Gbar | Y |
| X | 1 | 0 |
| 0 | 0 | A |
| 1 | 0 | B |

  

MUX 2X1- WITH DELAY CODE

```


module mux_enable(a,b,sel,gbar,y)
  input a,b,sel,gbar;
  output y;
  wire s1,s2,s3,s4,s5;
  time dly = 7; //simulation screen units
  assign #dly y=s4|s5;
  assign #dly s4=a & s2 & s1;
  assign #dly s5=b & s3 & s1;
  assign #dly s2= ~sel;
  assign #dly s3= ~s2;
  assign #dly s1= ~gbar;
endmodule
  
```

  

SIMULATION OF MUX 2X1

- If $T_0 = 100\text{ns}$
 - $T_1 = 114\text{ns}$, why?

```
assign #dly y=s4|s5;
assign #dly s4=a & s2 & s1;
assign #dly s5=b & s3 & s1;
assign #dly s2= ~sel;
assign #dly s3= ~s2;
assign #dly s1= ~gbar;
```

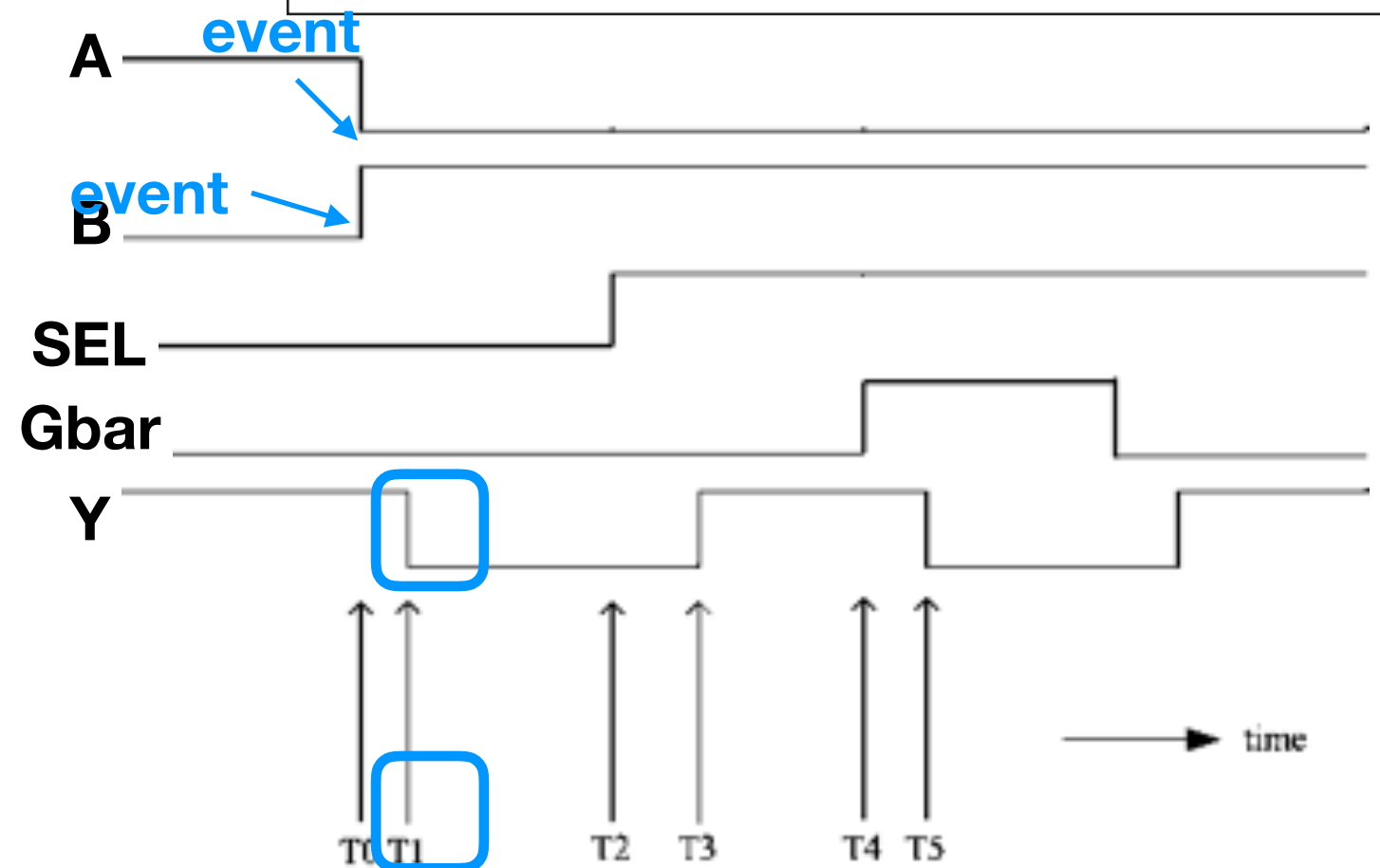


SIMULATION OF MUX 2X1

- If $T_0 = 100\text{ns}$
 - $T_1 = 114\text{ns}$, why?
- If $T_2 = 200\text{ns}$
 - $T_3 = 228\text{ns}$, why?

```


assign #dly y=s4|s5;
assign #dly s4=a & s2 & s1;
assign #dly s5=b & s3 & s1;
assign #dly s2= ~sel;
assign #dly s3= ~s2;
assign #dly s1= ~gbar;
    
```

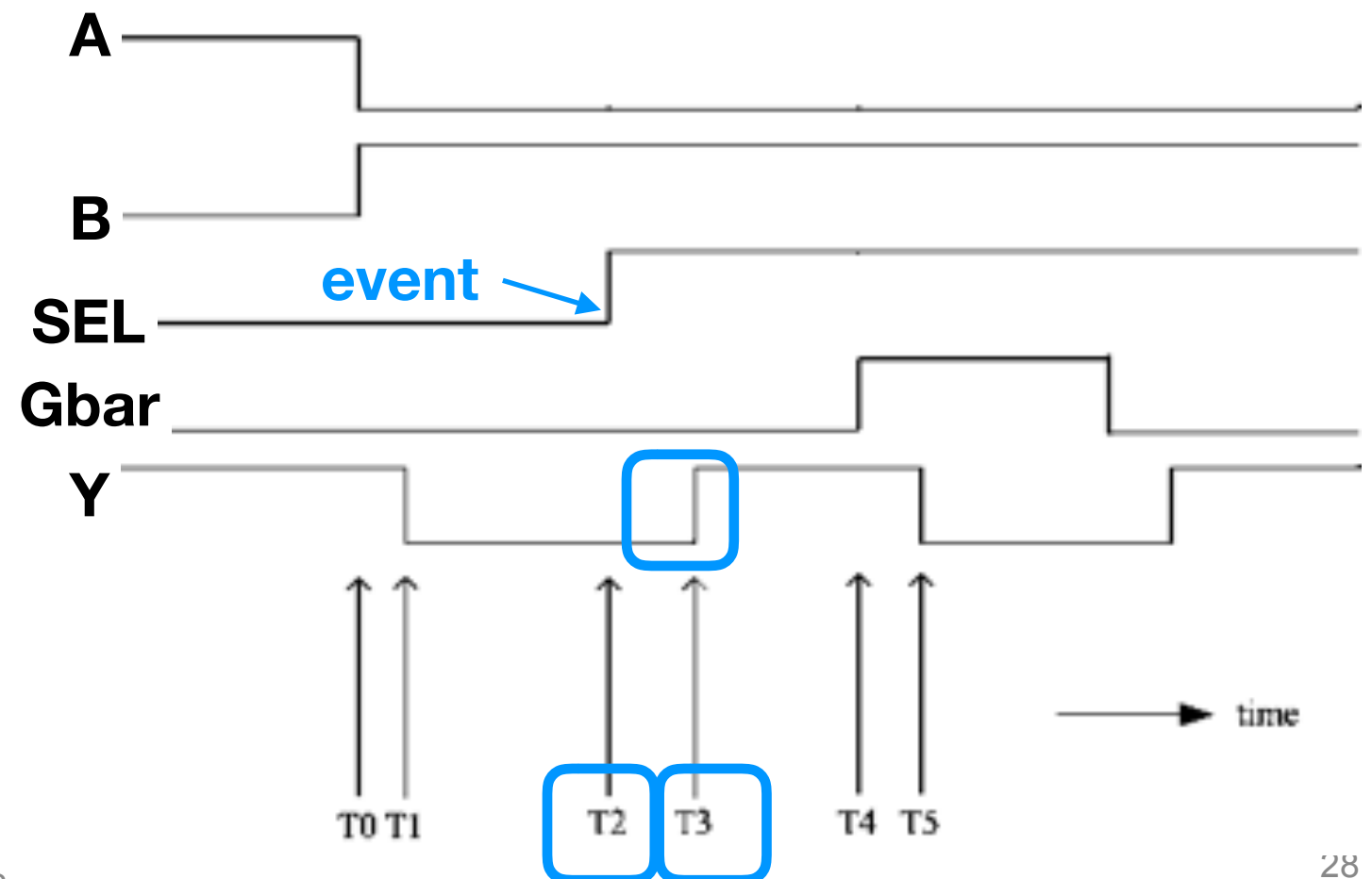

SIMULATION OF MUX 2X1

- If $T_0 = 100\text{ns}$
 - $T_1 = 114\text{ns}$, why?
- If $T_2 = 200\text{ns}$
 - $T_3 = 228\text{ns}$, why?
- If $T_4 = 300\text{ns}$
 - $T_5 = 321\text{ns}$, why?

```
assign #dly y=s4|s5;
assign #dly s4=a & s2 & s1;
assign #dly s5=b & s3 & s1;
assign #dly s2= ~sel;
assign #dly s3= ~s2;
assign #dly s1= ~gbar;
```

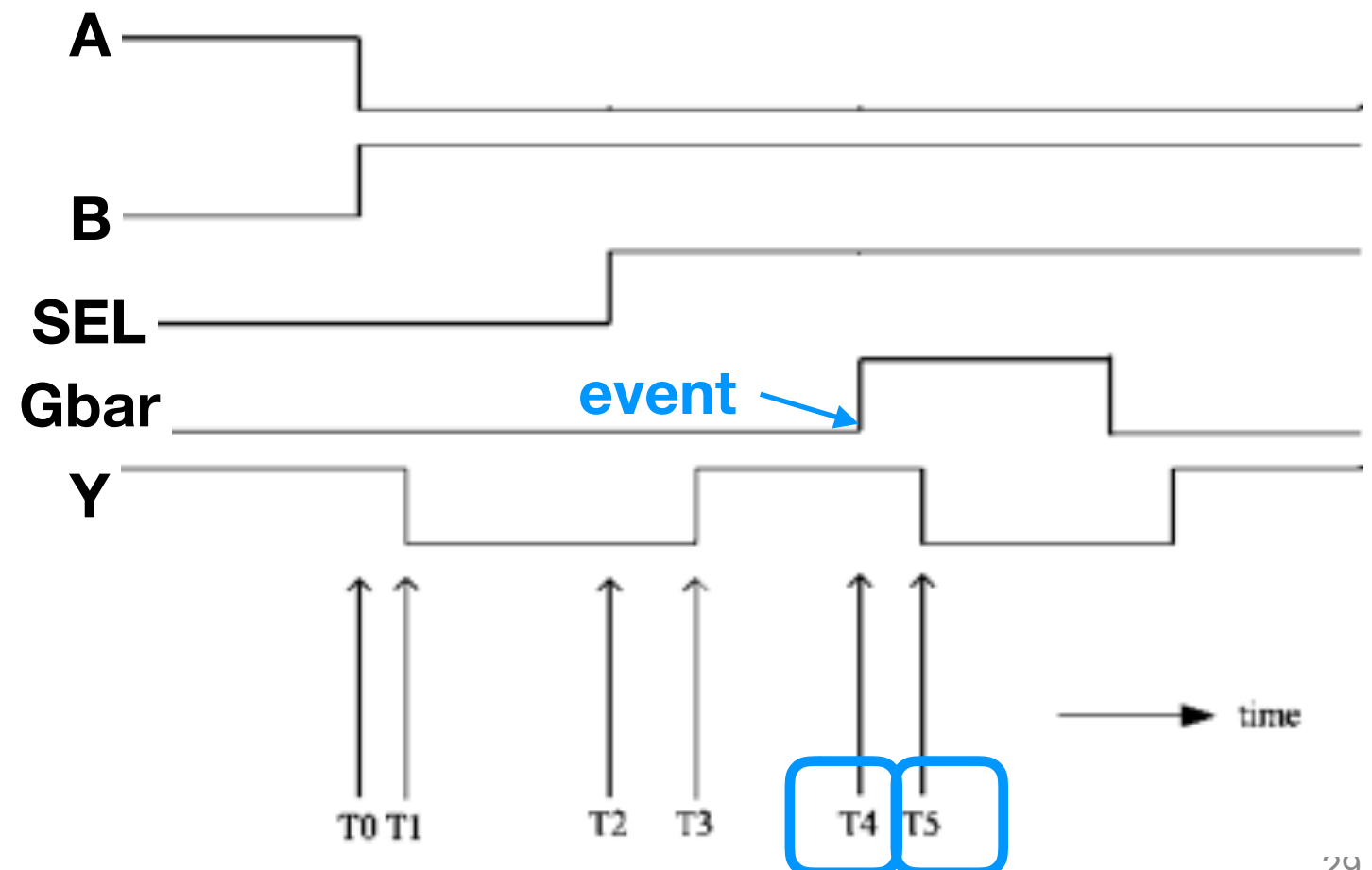

LECTURE 3: OVERVIEW

- Typical mistakes in Verilog
- Data flow description
- Concurrent signal assignment + examples
- Assignment with delay + examples
- Concurrent code Verilog

CONCURRENT IMPLEMENTATION

- Purely Concurrent Statement Syntax

- `assign`

- `assign out = in_a & in_b;`

- `? :`

- `mux = (addr==2'b00) ? i0 :
 ((addr == 2'b01) ? i1 :
 ((addr == 2'b10) ? i2 :
 ((addr == 2'b11) ? i3 :
 4'bz))) ;`

- `generate`

CONCURRENT IMPLEMENTATION: GENERATE

- **Syntax**

```
genvar i;
generate
for (i=0; i< MAX; i=i+1) begin
    [statements]
end
endgenerate
```


CONCURRENT IMPLEMENTATION: GENERATE

- Example on loop**

```
input [7:0] x;
```

```
input [15:0] y;
```

```
output [7:0] z;
```

```
genvar i;
```

```
generate
```

```
    for (i=0; i<=7; i=i+1) begin
```

```
        assign z[i] = x[i] & y[i+8];
```


```
    end
```

```
endgenerate
```

```
/*    Equivalent Example    */
assign z[0] = x[0] & y[0+8];
assign z[1] = x[1] & y[1+8];
assign z[2] = x[2] & y[2+8];
assign z[3] = x[3] & y[3+8];
assign z[4] = x[4] & y[4+8];
assign z[5] = x[5] & y[5+8];
assign z[6] = x[6] & y[6+8];
assign z[7] = x[7] & y[7+8];
```

CONCURRENT IMPLEMENTATION: PARITY DETECTOR

- XOR Tree**

 

```
module xor_tree( input [7:0]x, output y );
```

```
  wire [6:0] temp;
```

```
  assign temp[0] = x[0];
```

```
  assign temp[1] = temp[0] ^ x[1];
```

```
  assign temp[2] = temp[1] ^ x[2];
```

```
  assign temp[3] = temp[2] ^ x[3];
```

```
  assign temp[4] = temp[3] ^ x[4];
```

```
  assign temp[5] = temp[4] ^ x[5];
```

```
  assign temp[6] = temp[5] ^ x[6];
```


```
  assign y = temp[6] ^ x[7];
```

```
endmodule
```

$$y = x(0) \oplus x(1) \oplus x(2) \oplus \dots \oplus x(N-1)$$

CONCURRENT IMPLEMENTATION: PARITY DETECTOR

- Does this work?
- **NO**, why?

 

```
module xor_tree( input [7:0]x, output y );
```

```
  wire [6:0] temp;
```

```
  genvar i;
```

```
  generate
```

```
    for (i=1; i<7; i=i+1) begin
```

```
      assign temp[i] = temp[i-1] ^ x[i];
```

```
    end
```

```
  endgenerate
```


```
  assign y = temp[7];
```

```
endmodule
```

$$y = x(0) \oplus x(1) \oplus x(2) \oplus \dots \oplus x(N-1)$$

CONCURRENT IMPLEMENTATION: PARITY DETECTOR

- Does this work?
- YES

 

```
module xor_tree( input [7:0]x , output y );
```

```
  wire [6:0] temp;
```

```
  temp[0] = x[0];
```

```
  genvar i;
```

```
  generate
```

```
    for (i=1; i<7; i=i+1) begin
```

```
      assign temp[i] = temp[i-1] ^ x[i];
```

```
    end
```

```
  endgenerate
```


```
  assign y = temp[6] ^ x[7];
```

```
endmodule
```

$$y = x(0) \oplus x(1) \oplus x(2) \oplus \dots \oplus x(N-1)$$

CONCURRENT IMPLEMENTATION: PARITY DETECTOR

 - **Number of 1's in a signal**
 - Odd then PD = 1
 - Even then PD = 0



$$y = x(0) \oplus x(1) \oplus x(2) \oplus \dots \oplus x(N-1)$$

- **Usage**
 - Error detection methods
 - Even parity
 - Odd parity