

# EECS 31L: INTRODUCTION TO DIGITAL DESIGN LAB LECTURE 2

---

**Salma Elmalaki**  
**salma.elmalaki@uci.edu**

The Henry Samueli School of Engineering  
Electrical Engineering and Computer Science  
University of California, Irvine



# LECTURE 2: LOGISTICS

- Lab 1 deadline is Sunday 1/17/2021 at 11:00 pm on canvas
  - Late submission between 11:00pm to 11:59pm
  - Server closes immediately at midnight
- Lab 2 will be assigned on Monday 1/18/2021
  - You will have two weeks to finish it
- Monday 1/18 (MLK) - no lab session
  - Makeup: Extended OH for Maryam
  - You can attend any lab session this week

# LECTURE 2: OVERVIEW


- Deeper insight in Verilog structures with additional examples
- Verilog data types
- Verilog operators
- Some examples for concurrency
- Lab 2 description

# LECTURE 2: OVERVIEW

- Deeper insight in Verilog structures with additional examples
- Verilog data types
- Verilog operators
- Some examples for concurrency
- Lab 2 description
 
# VERILOG BASICS

- Each design in Verilog consists of one main part:



Circuit Ports (I/Os) (mandatory)

Generic constants (optional)

Other declaration (optional)

Structure 1

```
module module_name (port_name1, port_name2, ... );
    port_mode1 port_name1, port_name2;
    port_mode2 port_name3;
//body of module
endmodule
```


Structure 2

```
module module_name (port_mode1 port_name1,
port_name2, port_mode2 port_name3);
//body of module
endmodule
```


Note the semicolon at the end of the port list!
 
# VERILOG BASICS

- Each design in Verilog consists of one main part:



How to describe functionality?

 

What a module does

How a module is built


```
module identifier(port_list);
[ports_declaration]

//module_body

endmodule
```
 
# VERILOG BASICS: PORT MODES

- **input**: can only be read
- **output**: can be on either side of assignment
- **inout**: can be read or written (is a bidirectional bus)



# VERILOG BASICS: CONTINUOUS ASSIGNMENT STATEMENTS

## assign statement

Describes only combinational logic

These statements are re-evaluated anytime any of the inputs on the right hand side changes

`assign <out> = <in0> <operator> <in1> ... ;`

Example

`assign Y = A + B;`



# VERILOG BASICS: CONTINUOUS ASSIGNMENT STATEMENTS

Find the bug in this 2 input AND gate!

```
module assign_example (A,B,Y) ;
    input A;
    input B;
    output Y

    Y = A & B;
endmodule
```

# VERILOG BASICS: CONTINUOUS ASSIGNMENT STATEMENTS

Fixed version

```
module assign_example (A,B,Y) ;
    input A;
    input B;
    output Y;

    assign Y = A & B;
endmodule
```

# VERILOG CODE STRUCTURE EXAMPLE

## 4x1 multiplexer

```

module mux_4_1 (x0,x1,x2,x3,sel,y);
  input [7:0] x0,x1,x2,x3;
  input [1:0] sel;
  output [7:0] y;
  
```

Size (bit-width)


```

assign y = (sel==2'b00) ? x0:
             (sel==2'b01) ? x1:
             (sel==2'b10) ? x2:
             x3;
  
```

```

endmodule
  
```

sel <sub>1</sub>	sel <sub>0</sub>	Y
0	0	X <sub>0</sub>
0	1	X <sub>1</sub>
1	0	X <sub>2</sub>
1	1	X <sub>3</sub>

 

# VERILOG CODE STRUCTURE EXAMPLE

## 4x1 multiplexer

```
module mux_4_1 (x0,x1,x2,x3,sel,y);
  input [7:0] x0,x1,x2,x3;
  input [1:0] sel;
  output [7:0] y;
```


```
  assign y = (sel==2'b00) ? x0:
             (sel==2'b01) ? x1:
             (sel==2'b10) ? x2:
             x3;
```

/\* Or it can be written as case statement in  
always block or if statement (revise lecture 1  
behavioral structural)

\*/

```
endmodule
```

sel <sub>1</sub>	sel <sub>0</sub>	Y
0	0	X <sub>0</sub>
0	1	X <sub>1</sub>
1	0	X <sub>2</sub>
1	1	X <sub>3</sub>

 

# VERILOG CODE STRUCTURE EXAMPLE

```
module mux_4_1 (x0,x1,x2,x3,sel,y);
```

```
  input [7:0] x0,x1,x2,x3;
```

```
  input [1:0] sel;
```

```
  output [7:0] reg y;
```

```
  always @(x0,x1,x2,x3,sel) ←
```

```
  begin
```

```
    case (sel):
```

```
      2'b00:
```

```
        y = x0;
```

```
      2'b01:
```

```
        y = x1;
```

```
      2'b10:
```

```
        y = x2;
```

```
      2'b11:
```

```
        y = x3;
```

```
    endcase
```

```
  end
```


```
endmodule
```

Sensitivity list

Rule

assign statements  
cannot be used inside  
always block

sel <sub>1</sub>	sel <sub>0</sub>	Y
0	0	X <sub>0</sub>
0	1	X <sub>1</sub>
1	0	X <sub>2</sub>
1	1	X <sub>3</sub>

 

# VERILOG CODE STRUCTURE EXAMPLE

```
module mux_4_1 (x0,x1,x2,x3,sel,y);
```

```
  input [7:0] x0,x1,x2,x3;
```

```
  input [1:0] sel;
```

```
  output [7:0] reg y;
```

Sensitivity list

```
  always @(*)
```

```
  begin
```

```
    case (sel):
```

```
      2'b00:
```

```
        y = x0;
```

```
      2'b01:
```

```
        y = x1;
```

```
      2'b10:
```

```
        y = x2;
```

```
      2'b11:
```

```
        y = x3;
```

Rule


assign statements  
cannot be used inside  
always block

```
    endcase
```

```
  end
```

```
endmodule
```

sel <sub>1</sub>	sel <sub>0</sub>	Y
0	0	X <sub>0</sub>
0	1	X <sub>1</sub>
1	0	X <sub>2</sub>
1	1	X <sub>3</sub>

 

# VERILOG DATA TYPES

**-Net**

**-Register**

**-Vectors (Defined and accessed by brackets)**

- multi-bit words of type reg or net (wire)

**-Integer**

- Defined by predefined word integer

**-Real**

- Defined by predefined word real

**-Parameter**

- Define global constants
- Defined by predefined word parameter

**-Array (Defined and accessed by brackets)**

- Arrays for integer, time, reg, and vectors of reg

# VERILOG DATA TYPES

4-state types

## •Nets

- Defined by predefined word *wire*, with 4 known values
- Can be driven in concurrent statements
- They change continuously by circuit
- Syntax: Example:

```
wire net_name; //just name
wire S1= 1'b0; //name and initial value
```

Value	Definition
0	Logic 0 (false)
1	Logic 1 (true)
X	Unknown
Z	High impedance

## •Registers


- Defined by predefined word *reg*, with 4 known values
- Can be driven in sequential statements
- In contrast to nets stores values until they are updated
- Syntax: Example:

```
reg reg_name; //just name
reg S1= 1'b0; //name and initial values
```



# VERILOG DATA TYPES

Example

 

```

module always_ex(A,B,C,Y);
    input A;
    input B;
    input C;
  
```

**endmodule**


```

module assign_ex(A,B,C,Y);
    input A;
    input B;
    input C;
  
```

**endmodule**

# VERILOG DATA TYPES

Example

 

```

module always_ex(A,B,C,Y);
    input A;
    input B;
    input C;
    output reg Y;
  
```

**endmodule**


```

module assign_ex(A,B,C,Y);
    input A;
    input B;
    input C;
    output Y;
  
```

**endmodule**

# VERILOG DATA TYPES

Example

 

```

module always_ex(A,B,C,Y);
    input A;
    input B;
    input C;
    output reg Y;

    reg interm;
  
```

**endmodule**

```


module assign_ex(A,B,C,Y);
    input A;
    input B;
    input C;
    output Y;

    wire interm;
  
```

**endmodule**

# VERILOG DATA TYPES

Example

 

```

module always_ex(A,B,C,Y);
  input A;
  input B;
  input C;
  output reg Y;

  reg interm;

  always @(*) begin
    interm = A & B;
    Y      = ~interm | C;
  end
endmodule
  
```

=

```

module assign_ex(A,B,C,Y);
  input A;
  input B;
  input C;
  output Y;

  wire interm;

  assign interm = A & B;
  assign Y      = ~interm | C;

endmodule
  
```

# VERILOG DATA TYPES

## •Vector

Multiple bits.

A reg or a net can be declared as a vector.

Vectors are declared by brackets [ ]

Examples:

```
reg [7:0] MB1; //8-bit reg vector with MSB=7 LSB=0
wire [0:7] MB2; //8-bit wire vector with MSB=0 LSB=7
reg [3:0] bitslice;
// with initialization
wire [3:0] multiBitWord1 = 4'b1010;
reg [7:0] total = 8'd12; //8 bits and decimal value 12
                        // 8'b0000_1100
```

## Referencing vectors

```
a = multiBitWord1[3]; // a = 1
bitslice1 = total[3:0]; // bitslice1 = 4'b1100
bitslice2 = total[7:4]; // bitslice2 = 4'b0000
```

# VERILOG DATA TYPES

## •Vector

Multiple bits.

A reg or a net can be declared as a vector.

Vectors are declared by brackets [ ]

Examples:

```
reg [7:0] MB1; //8-bit reg vector with MSB=7 LSB=0
wire [0:7] MB2; //8-bit wire vector with MSB=0 LSB=7
reg [3:0] bitslice;
```

## •Array

Array as per definition in a collection of elements of same type.


```
reg signed [3:0] anArray [0:4];
//anArray has 5 elements and each element is 4 signed bits
```

Size of each element


Size of the array
 
# VERILOG DATA TYPES

```
//An 4-bit vector
wire [3:0] areg;
```



 
```
//A memory of 4 one-bit elements
reg amem [0:3];
```



 
# VERILOG DATA TYPES


```
//An 4-bit vector
wire [3:0] areg;
```



 
```
//A memory of 4 one-bit elements
reg amem [0:3];
```


 
```
//A memory of four 6-bit
reg [0:5] bmem [3:0];
```



 
```
//A two dimensional memory of one-bit elements
reg cmem [3:0][2:0];
```





 
# VERILOG DATA TYPES


```
//An 4-bit vector
wire [3:0] areg;
```



 
```
//A memory of 4 one-bit elements
reg amem [0:3];
```


 
```
//A memory of four 6-bit
reg [0:5] bmem [3:0];
```


 
```
//A two dimensional memory of one-bit elements
reg cmem [3:0] [2:0];
```




# VERILOG DATA TYPES

## •Parameter


//An 4-bit vector

wire [3:0] areg;

 


//A memory of 4 one-bit elements

reg amem [0:3];

 


//A memory of four 6-bit

reg [0:5] bmem [3:0];

 

//A two dimensional memory of one-bit elements

reg cmem [3:0][2:0];

 

# VERILOG DATA TYPES

## •Parameter

Represents a global constant

Declared by a predefined word *parameter*

Example:

```
parameter N = 3;
```

```
//An 4-bit vector
```

```
wire [N:0] areg;
```

```
//A memory of 4 one-bit elements
```

```
reg amem [0:N];
```

```
//A memory of four 6-bit
```

```
reg [0:5] bmem [N:0];
```

```
//A two dimensional memory of one-bit elements
```

```
reg cmem [N:0][2:0];
```

# LECTURE 2: OVERVIEW

- Deeper insight in Verilog structures with additional examples
- Verilog data types
- Verilog operators
- Some examples for concurrency
- Lab 2 description

# OPERATORS

- Logical operators
  - Such as AND, OR, XOR, ...
- Relational
  - Compare relation between objects
  - Such as less than, equal, greater than or equal, ...
- Arithmetic operators
  - Such as addition and subtraction
- Shift operators
  - Move bits of an object to a certain direction

# BITWISE LOGICAL OPERATORS

- Single operand or multiple operands
- The operand(s) has(have) single or multiple bits
- Example

If A = "0101", B = "1100"

C = A ^ B      D = A & B

means C = "1001"

means D = "0100"

Operation	Verilog
AND	&
OR	
NAND	~(&)
NOR	~( )
XOR	^
XNOR	~(^)
NOT	~

# BITWISE LOGICAL OPERATORS

## Reduction logical operators

- Need a single operand
- The result is a Boolean variable
- Example:
  - If  $x = "1010"$
  - $y = \&x$      //  $y = (1 \& 0 \& 1 \& 0)$
  - $y = |x$      //  $y = (1 | 0 | 1 | 0)$
  - $y = \sim\&x$    //  $y = (1 \sim\& 0 \sim\& 1 \sim\& 0)$

# BITWISE LOGICAL OPERATORS

## Reduction logical operators

- Need a single operand
- The result is a Boolean variable
- Example:
  - If  $x = "1010"$
  - $y = \&x$      //  $y = (1 \& 0 \& 1 \& 0)$
  - $y = |x$      //  $y = (1 | 0 | 1 | 0)$
  - $y = \sim\&x$    //  $y = (1 \sim\& 0 \sim\& 1 \sim\& 0)$

Operand	$\&$	$\sim\&$	$ $	$\sim $	$\wedge$	$\sim\wedge$	Comments
4'b0000	0	1	0	1	0	1	No bits set
4'b1111	1	0	1	0	0	1	All bits set
4'b0110	0	1	1	0	0	1	Even number of bits set
4'b1000	0	1	1	0	1	0	Odd number of bits set



# BITWISE LOGICAL OPERATORS

## Reduction logical operators

- Need a single operand
- The result is a Boolean variable
- Example:
  - If  $x = "1010"$
  - $y = \&x$  //  $y = (1 \& 0 \& 1 \& 0)$
  - $y = |x$  //  $y = (1 | 0 | 1 | 0)$
  - $y = \sim\&x$  //  $y = (1 \sim\& 0 \sim\& 1 \sim\& 0)$

Operand	$\&$	$\sim\&$	$ $	$\sim $	$\wedge$	$\sim\wedge$	Comments
4'b0000	0	1	0	1	0	1	No bits set
4'b1111	1	0	1	0	0	1	All bits set
4'b0110	0	1	1	0	0	1	Even number of bits set
4'b1000	0	1	1	0	1	0	Odd number of bits set

# BOOLEAN LOGICAL OPERATORS

- Need at least two operands
- Return Boolean type value
  - false (0)
  - true (non-zero)
- More than one condition can be checked

Examples:

If (cond1 && cond2) ....

Operation	Verilog
and	&&
or	
not	!

# RELATIONAL OPERATORS

The result of these operators are Boolean

- (in)equality
  - It compares 2 values(1,0)
    - The result is unknown (x) if operand are other than 1 and 0
  - Bit by bit comparison
  - If result of condition expression is x
    - Both true and false parts are executed
- (in)equality inclusive
  - It compares all 4 values(1,0,x,z)

Operation	Verilog
Equality	==
Inequality	!=
Less than	<
less than or equal	>=
greater than	>
greater than or equal	>=
equality inclusive	===
inequality inclusive	!==

# ARITHMETIC OPERATORS

**C = A operation B**

Description	Operator	A and B types	Y type
add, sub, multiplication, division,	+ , - , * , /	A numeric B numeric	numeric
Modulus	mod	A numeric (not real) B numeric (not real)	numeric (not real)
Exponent	**	A numeric B numeric	numeric
concatenation	{ , } <sup>1</sup>	A numeric or array B numeric or array	Same as A
Repetition	{N{A}} <sup>1</sup>	A numeric or array	Same as A

```
reg a = 1'b1; reg b = 2'b00
y = { 4{a}, 2{b} } // y = 8'b11110000
```

# SHIFT OPERATORS

$C = A \text{ shift\_operation } 1$

	Verilog	C (before)	C (after)
Shift logic left –fills with 0	$A \ll 1$	1010	0100
Shift logic right -fills with 0	$A \gg 1$	1010	0101
Shift arithmetic left - fills with LSB	$A \lll 1$	1001	0011
Shift arithmetic right - fills with MSB	$A \ggg 1$	1010	1101

**Red font** shows the location of same bit before and after shift

**Green font** shows the location of new values which is added to the empty location after shifting

Break 10 minutes



# LECTURE 2: OVERVIEW

- Deeper insight in Verilog structures with additional examples
- Verilog data types
- Verilog operators
- Some examples for concurrency
- Lab 2 description

# CONCURRENCY

```


module gates (input [3:0] a, b, output [3:0] y1, y2, y3,
y4, y5);

/* five different two-input logic gates acting on 4-bit
buses */

assign y1=a&b;           //AND
assign y2=a|b;           //OR
assign y3=a^b;           //XOR
assign y4 = ~(a & b);    // NAND
assign y5 = ~(a | b);    // NOR

endmodule

```

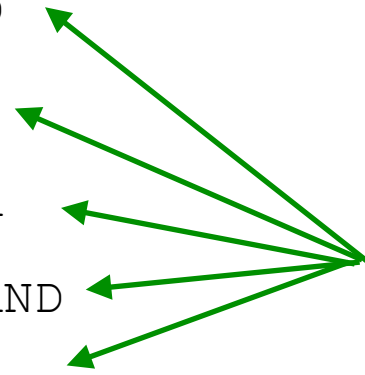

**Concurrent statements**



# CONCURRENCY

```
module and8 ( input [7:0] a, output y, z);

    assign y = &a;

    assign z = a[7] & a[6] & a[5] & a[4] & a[3] & a[2] & a[1] & a[0];

endmodule
```

What can you say about the value of y and z?

Both y and z outputs hold the same result


# CONCURRENCY

Suppose that mux2to1 module is already defined

```
module mux2to1(d0, d1, s, y);
input [3:0] d0, d1;
input s;
output [3:0] y;
// module body
endmodule

module mux4to1(x0, x1, x2, x3, s, y);
input [3:0] x0, x1, x2, x3;
input [1:0] s;
output [3:0] y;
wire [3:0] low, high;
mux2to1 lowmux (x0, x1, s[0], low);
mux2to1 highmux (x2, x3, s[0], high);
mux2to1 finalmux(low, high, s[1], y);
endmodule
```

sel <sub>1</sub>	sel <sub>0</sub>	Y
0	0	X <sub>0</sub>
0	1	X <sub>1</sub>
1	0	X <sub>2</sub>
1	1	X <sub>3</sub>

 

# LECTURE 2: OVERVIEW

- Deeper insight in Verilog structures with additional examples
- Verilog data types
- Verilog operators
- Some examples for concurrency
- Lab 2 description

# LECTURE 2: LAB 2

- Design an **ALU (Arithmetic Logic Unit)** module in Verilog
  - Modularity is essential to the success of large design
    - Remember 4to1 mux from 2to1 mux
  - Use what you learned here about mux to choose between different operations
  - Think about concurrency to make it efficient
- Make sure to attend the lab sessions for more explanation on the lab manual